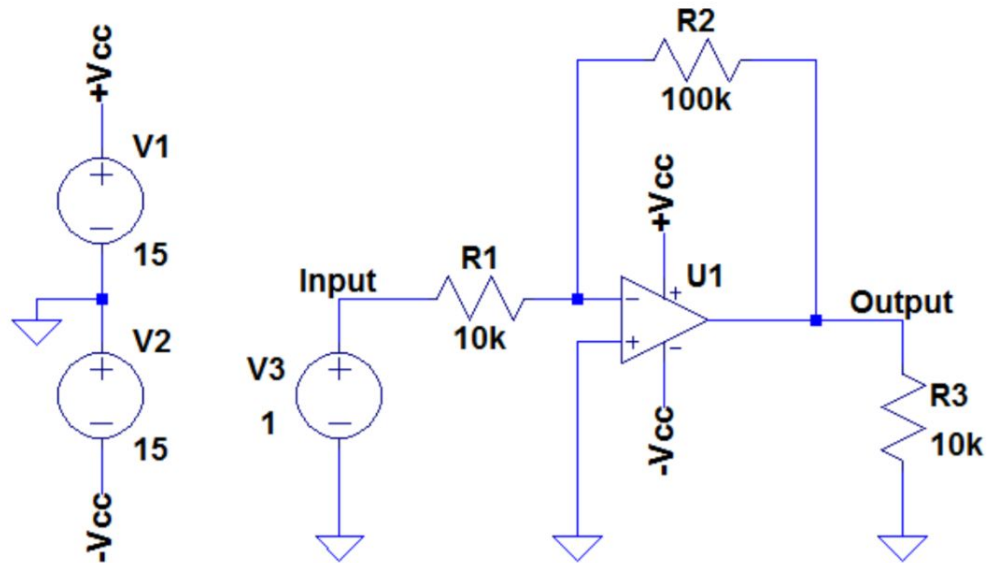



# Circuits Lab 11 4/8/2020 Chase Mulder

1. Make this circuit



- 2.



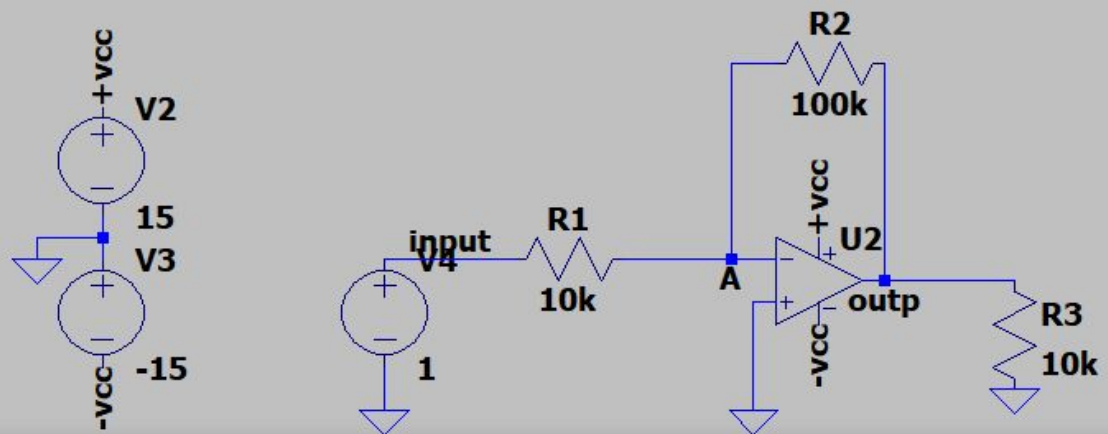

\* C:\Users\ickysaladtosser\Desktop\Circuits\ltpamp.asc


--- Operating Point ---

V(a):	1.81929	voltage
V(input):	1	voltage
V(-vcc):	15	voltage
V(+vcc):	15	voltage
V(outp):	10.0095	voltage
I(R3):	0.00100095	device_current
I(R2):	8.19022e-05	device_current
I(R1):	8.19285e-05	device_current
I(V4):	8.19285e-05	device_current
I(V2):	-0.000331286	device_current
I(V3):	0.000751673	device_current
Ix(u2:1):	-3e-08	subckt_current
Ix(u2:2):	-2.63614e-08	subckt_current
Ix(u2:3):	0.000331286	subckt_current
Ix(u2:4):	0.000751673	subckt_current
Ix(u2:5):	-0.00108285	subckt_current


3.



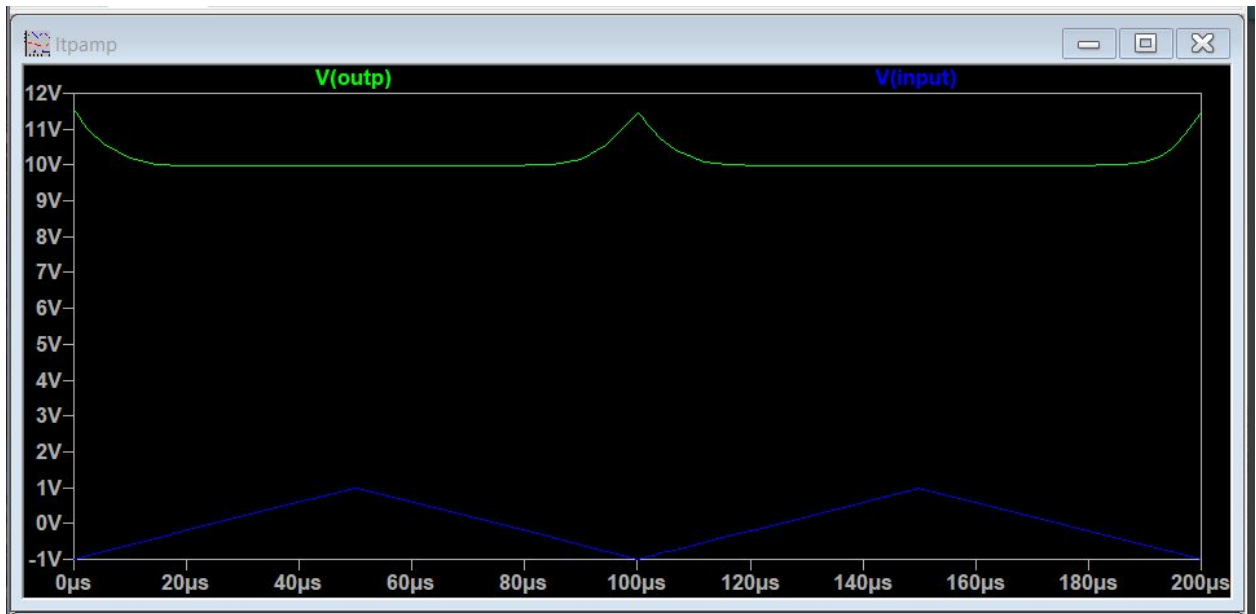
- 4.
5. To explain the above graph
  - a. Red line is the gain and the gain is  $V_{outp}/V_{input}$
  - b. Green in  $V_{input}$
  - c. Blue is  $V_{outp}$




- 6.

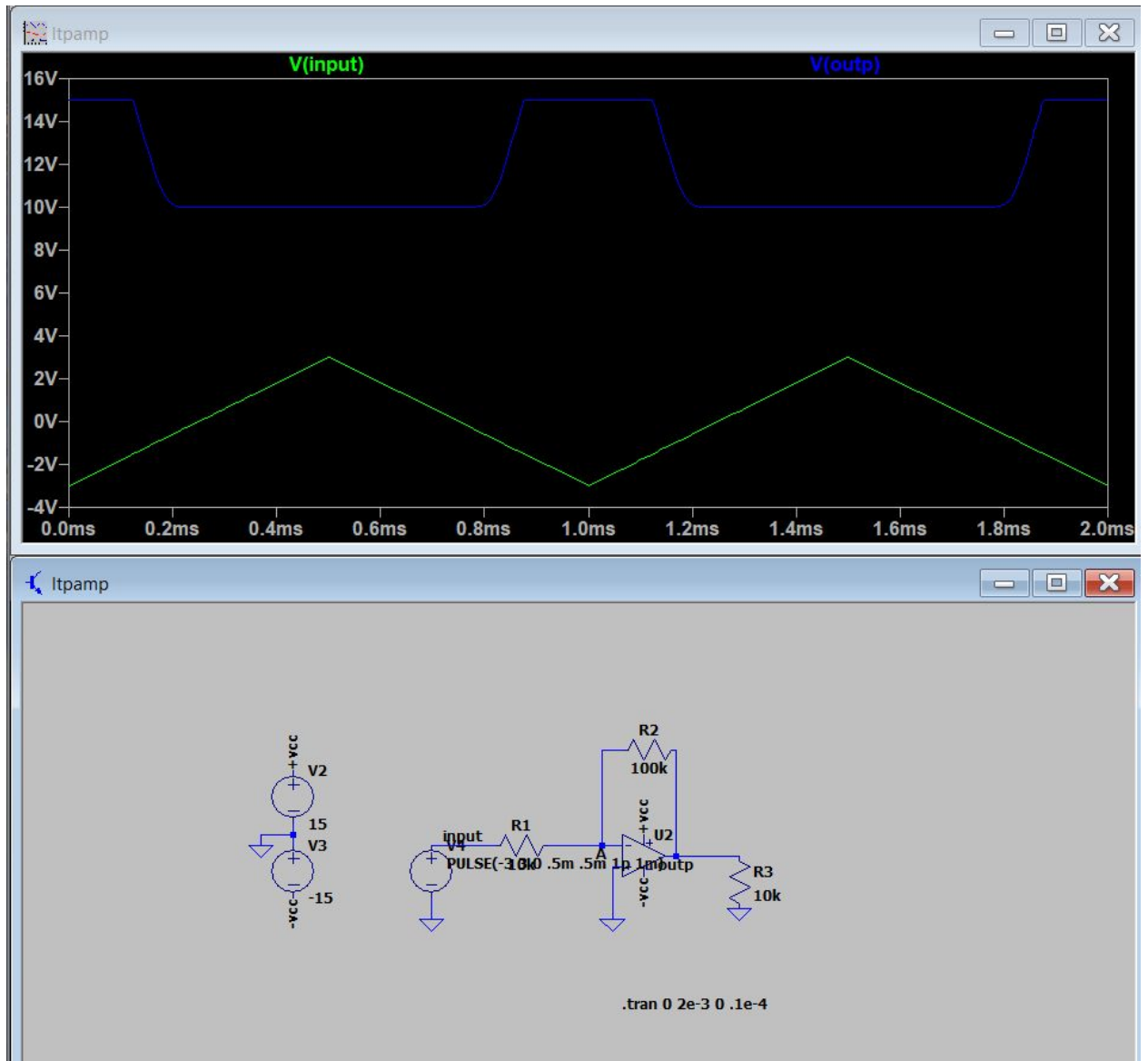

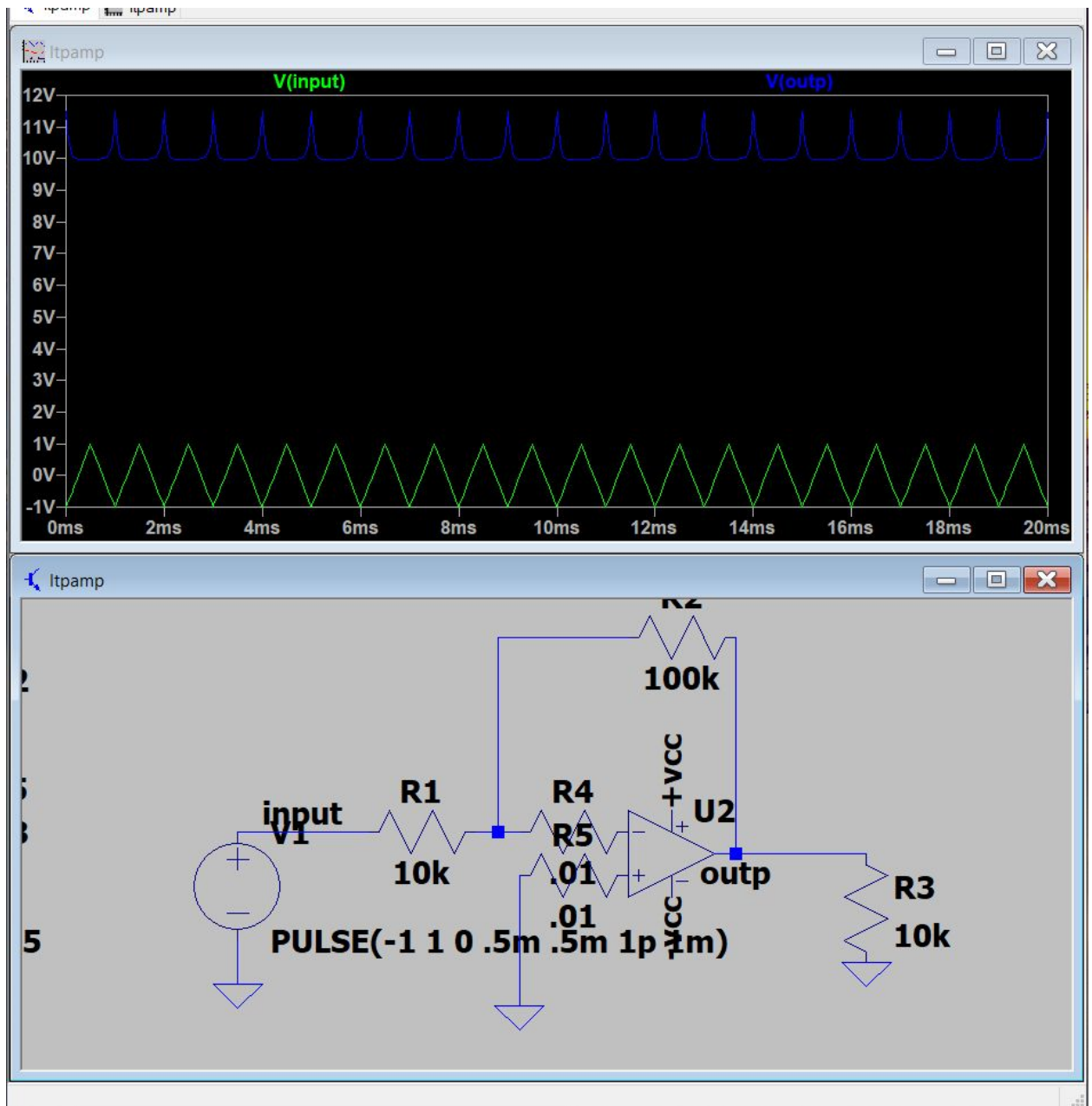
- 7.
8. R3 does not affect the gain of the op amp circuit because it's not RF or RS, R2 and R1 affect the gain.



9.

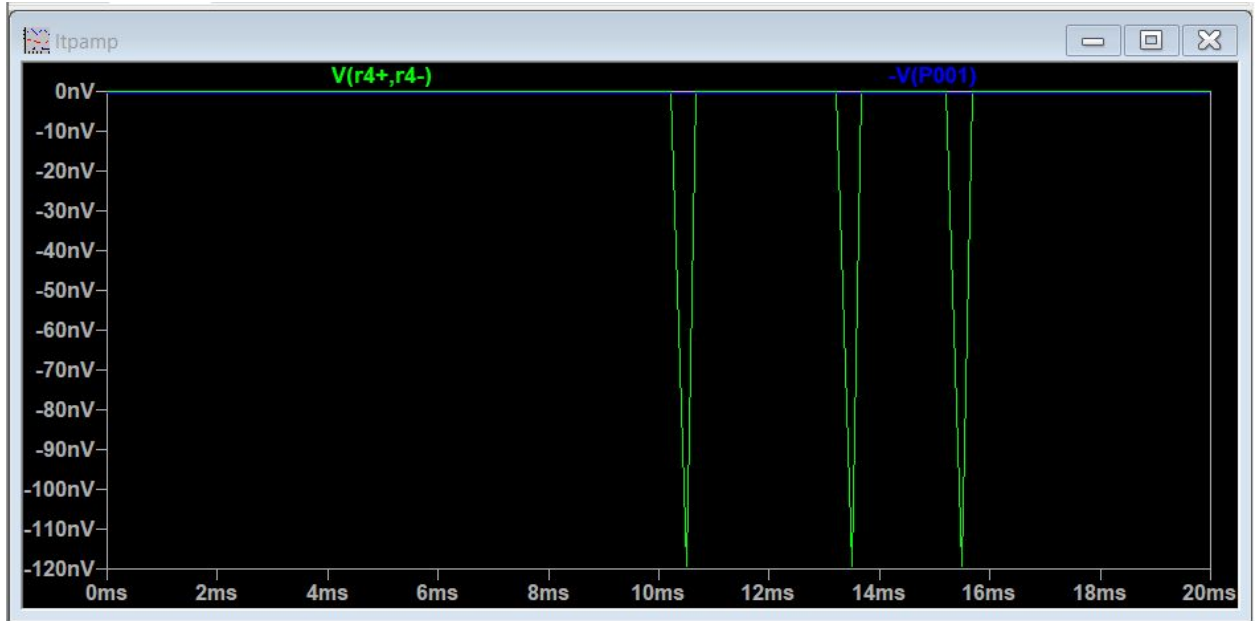

10.

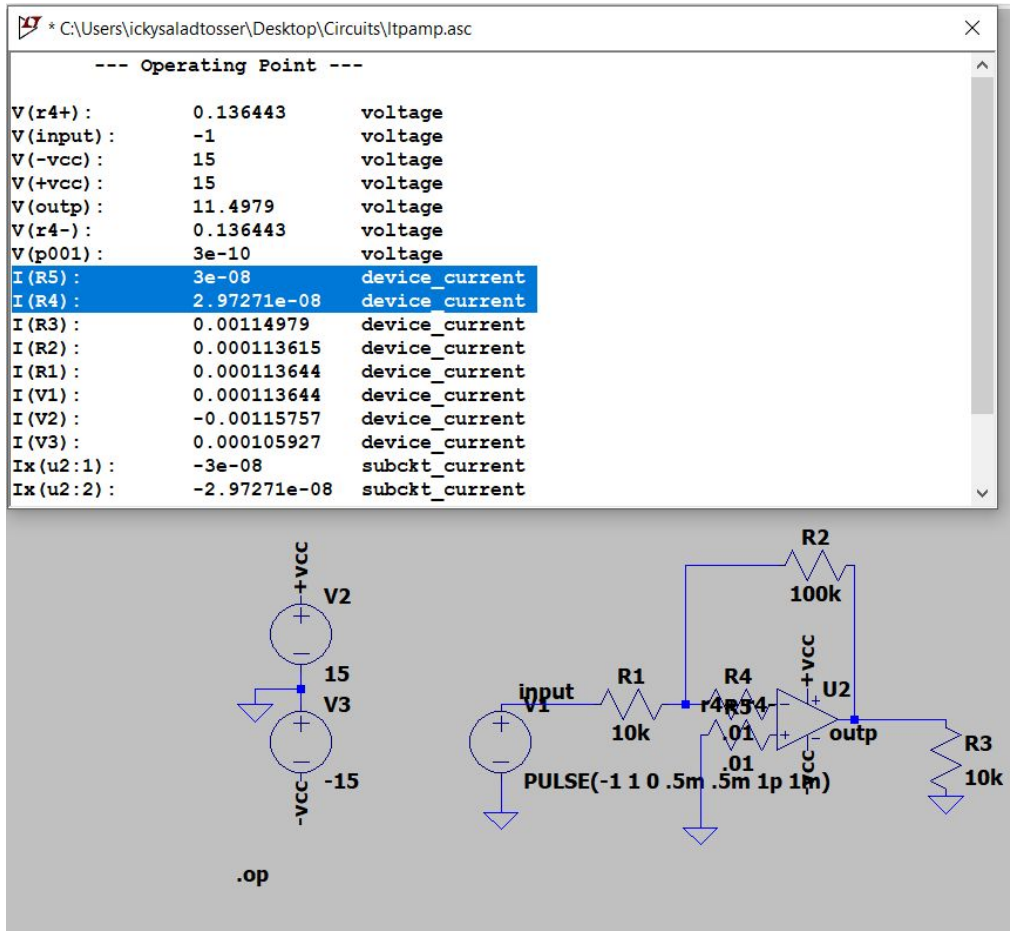


11.


For a non-inverting amp, the gain is:

$$\text{Gain} = 1 + (R2/R1)$$

12.

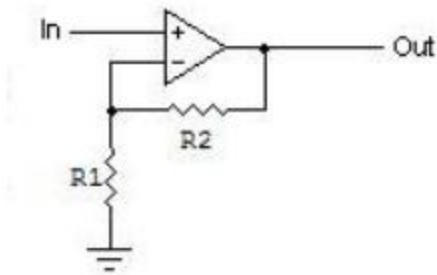

13.

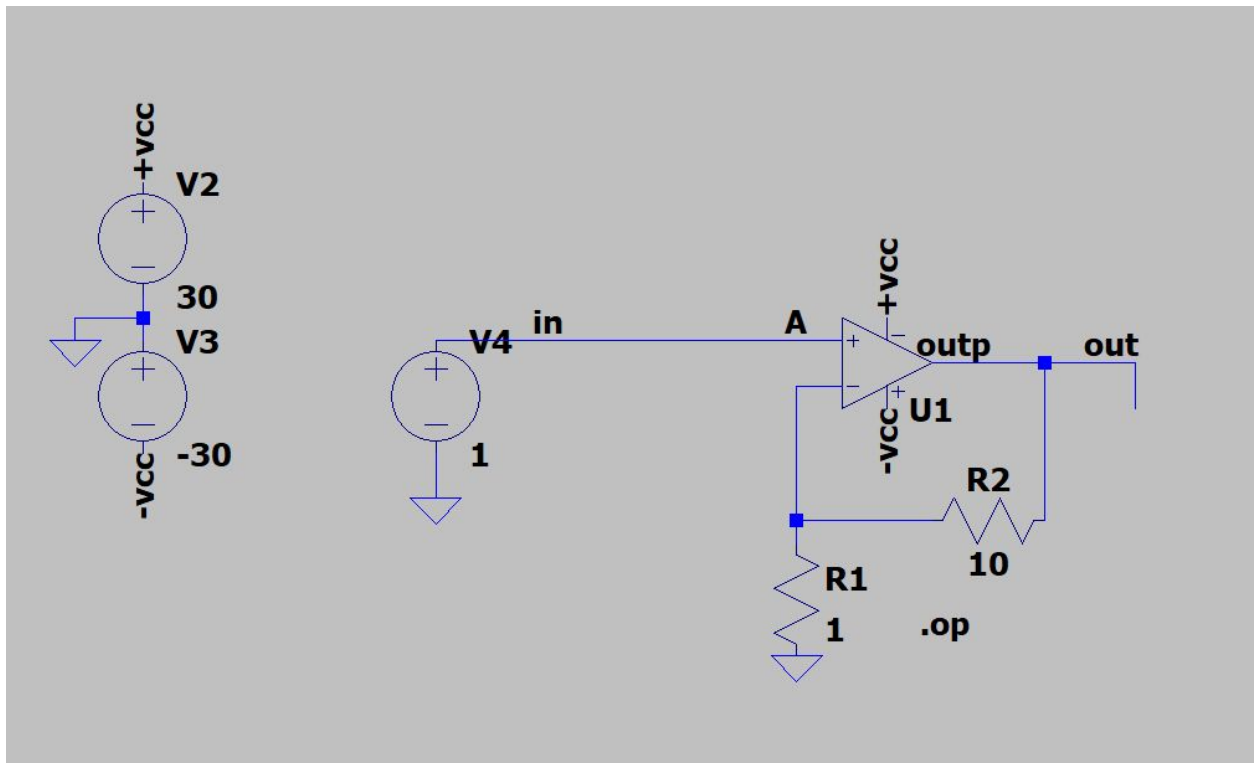

14.


15. This circuit should have a gain of 11

16. Gain 11 means a one volt in equals 11 volts out

17. Technically we'd need another inverting op amp because the vout will be -11

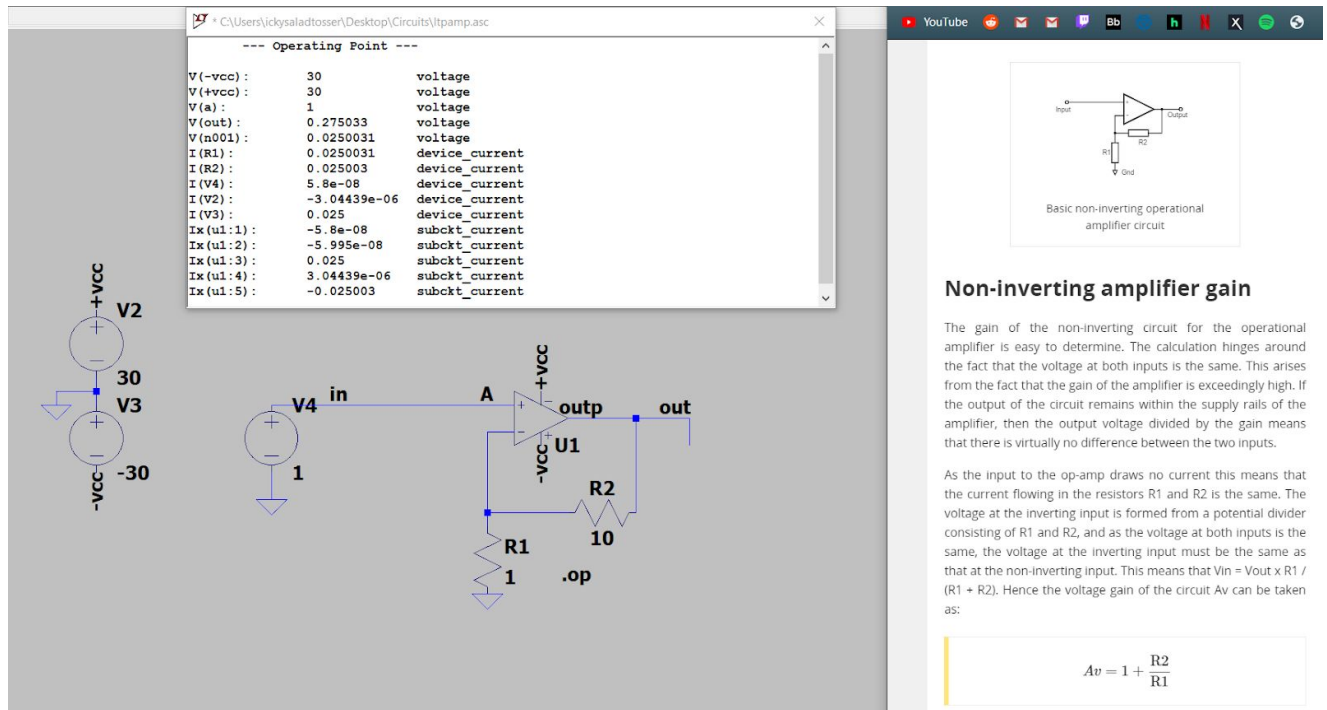18. Conclusion

- Op amp doesn't violate kcl. The saturation in the op amp is what is creating the current.
- Part 1 step 8 we found there's almost no current flowing into the op amp.  $V=IR$ , so having almost no current would result in very little voltage. If this current was 0 then we'd have a virtual short.
- How well did the 11V/V non inverting op amp do?



- d. The non inverting op amp with gain of 11 is not simulating in LTSpice properly, but the hand calculation on paper checks out with a non inverting op amp circuit found on the internet. In the circuit  $R2/R1 + 1$  will give the gain of the circuit. The values chosen for R2 is 10 ohms and R1 is 1ohm because  $10/1 = 10$  then +1 equals 11 gain voltage. I'm a little confused as to why the LT simulation is failing, but I have a suspicion it's to do with the rails +vcc and -vcc. In a non inverting op amp circuit the rail will be the output, so if a 1v comes in then the positive rail will be the output.